

FEEDBACK CIRCUIT CLAMPS PRECISELY

by Jerald Graeme, (602) 746-7412

A limiter circuit consisting of an input buffer (A_1), an output-scaling amplifier (A_2), two zener diodes (Z_1 and Z_2), and several other components can supply sharp, precise, bipolar clamp levels with continuous variable control, from 0 to $\pm 11V$. See Figure 1. A feedback loop enclosing the amplifiers and zeners generates the high clamping accuracy.

Within the limit range of the clamp ($\pm V_L$), the zener diodes are off, and A_2 feeds back its output to the inverting input of A_1 through R_4 . At the same time A_1 drives A_2 through the voltage divider R_V . The feedback forces the inverting input of op amp A_1 to equal E_I at the noninverting input terminal.

The circuit forces the inverting input of A_2 also to follow E_I . There's no signal voltage drop across R_4 , because no current can flow from it into A_2 's inverting input. Consequently, the noninverting input of A_2 , which defines the potentiometer output at feedback equilibrium, must also track E_I . A resistor voltage divider can replace the control potentiometer R_V in fixed-level limiting applications.

Amplifier A_2 then delivers an output:

$$E_O = (1 + R_3/R_2) E_I$$

when

$$-V_L < E_O < V_L$$

and

$$V_L = x [(1 + R_3/R_2)] (V_Z + V_F)$$

where x is the setting fraction of R_V , and V_Z and V_F are the zener and forward voltages, respectively. The overall circuit response, then, is simply that of a voltage amplifier when the output signal is within the limit boundaries.

Amplifier A_1 generates small deviations from an ideal response because A_2 's circuit gain $(1 + R_3/R_2)$ amplifies any offset voltage and noise from A_1 . Similarly, this loop gain mitigates the clamping error by sharpening its clamping response. The zener drive increases during the transition to the clamping state.

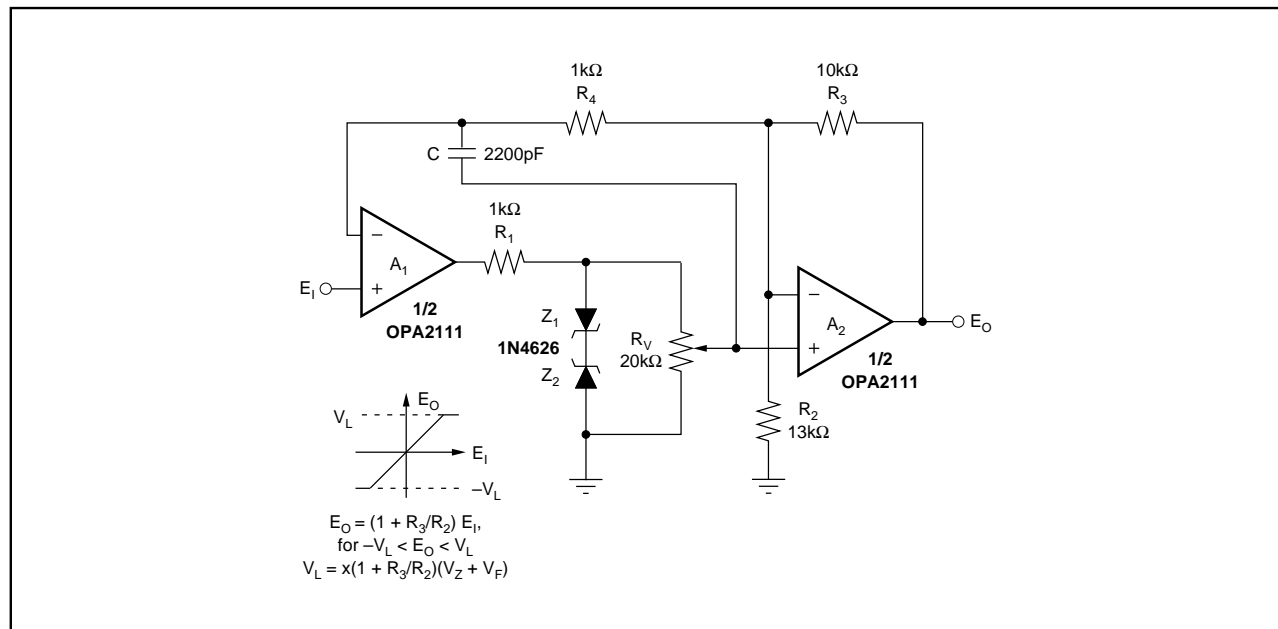


FIGURE 1. Amplifier A_1 Buffers and Amplifier A_2 Scales Input Signals Under Feedback Control. Zener diodes and a potentiometer or voltage divider in the feedback loop supply a continuously variable bipolar-clamping limit.

In the clamping mode, when the voltage across the two zeners reaches $\pm(V_Z + V_F)$, the circuit goes from acting as a voltage amplifier to acting as a voltage reference; the voltage across R_V is fixed and the potentiometer output is $\pm x(V_Z + V_F)$. Further increase in the magnitude of the signal at E_1 can't change this potentiometer value until it drops below the limit point V_L .

Thus, clamping is no longer limited to the fixed levels of available zener voltages. Even clamping levels as low as 5mV become practical when offset-trimmable OPA111 op amps replace the OPA2111. However, available zener voltages and the closed-loop gain of A_2 set the maximum clamping level.

Use of 10-V zeners and a gain of one for A_2 can cover the voltage range of most analog-signal processing. Unfortunately, the voltage temperature coefficients of 10-V zeners would produce thermal drift in the clamping level. With 5.6-V zeners, however, the temperature coefficients of the zener and forward voltages tend to cancel. For such zener

diodes $V_Z + V_F = 6.2V$, and the net drift is near zero. Then, with A_2 set to a gain of 1.77, the maximum limit voltage V_L is 11V.

The 5% tolerances of the zener voltages determine the basic accuracy of the clamp levels. The gain-setting resistors R_2 and R_3 impose additional tolerance error. However, adjusting the gain with these resistors can compensate for any zener-voltage error and resistor tolerances. With matched zeners, the adjustment can readily reduce the clamp-level errors to less than 1%. Without matching, the 5% error of simple zener clamping prevails, but the circuit still clamps sharply.

For frequency stability, resistor R_4 and capacitor C supply a frequency roll-off in A_1 . At high frequencies, the capacitor shorts the output of A_1 to its inverting input. Then A_1 and A_2 operate with independent feedback loops, and the overall circuit requires stability in the individual amplifiers.